

My Nixie Clock Project

by *Peter H. Wendt*

Rel. 0.9.5_en, Last Update: Wednesday, 2009-11-18

Most common question: "Your *what* Clock Project ?"

Before Light-Emitting Diodes (LEDs) and Liquid Crystal Displays (LCDs) the electronic industry used cold-cathode tubes for displaying numbers, symbols and even characters. Even though they are called "tubes" they differ from "radio tubes" by having no heater wire to heat the cathode - and therefore run much colder. They do have a glass envelope but unlike to (most) tubes they are not empty: they are filled with a gas compound, mainly neon gas. If you apply a voltage between the anode (+ pole) and one of the cathodes (- poles) the character-shaped cathode is covered with a pink to orange discharge glow.

"NIXIE" was a trademark from Burroughs Corp. for their numeric display tubes. It is rumoured that they invented this kind of tube - or at least they got patents for it. There were many different types of these tubes: viewed from the side, viewed from the top, small ones, big ones, giant sized, types where a neon glows through a character-shaped mask and arrays of multiple nixies with multiplexed wires. Even early "multi-segment" types were available, capable to display letters like the later LED 7-segment arrays.

The animation below shows the button-like, top-viewed ZM1020.
It is a Nixie with 15 mm (0.6") character height.




You got the idea, right ?
Now for some technical theory.

Basically these Nixie tubes are very simple devices. The following schematic will explain, how they work.

Nixie Tubes

Principle of Operation

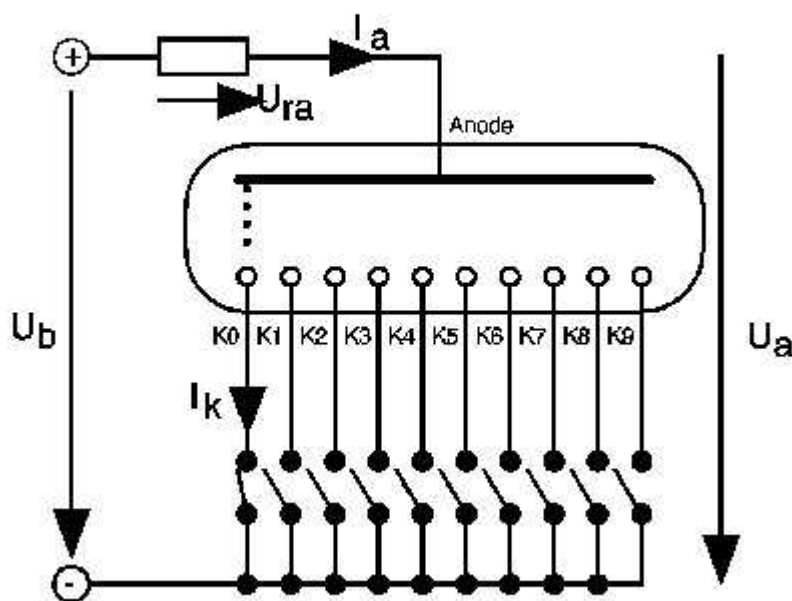

If you apply a voltage U_b the voltage drops across the current-limiting resistor when one of the cathodes K0 - K9 is tied to GND. The corresponding number-shaped cathode is then covered with a pink to orange glow. The values for the minimum U_b , the anode voltage U_a and the cathode current I_k needs to be taken from the nixie tube datasheet, but you can estimate 140 VDC for U_a and 2 mA for I_k as good starting values for most nixies.

If your U_b is about 220 VDC a 47K resistor / 0.5 Watts will do for some testings.

The [datasheet for the very common ZM1080 / 1082](#) says that U_b should be at least 170 VDC and the I_k should settle at around 2 mA. U_a will then establish at about 140 VDC "maintaining" voltage (noted as V_m in the datasheet). The difference between U_b and U_a is the U_{ra} that drops across the limiting resistor.

For a simplification we assume that the anode current I_a is equal to the cathode current I_k - you will have to tie only **one** cathode pin to GND at one time anyway. Nixies that use a "primer current" for faster ignition response have uneven anode and cathode currents. But we may leave that aside here.

Advantage: If you rig a multimeter in Milli-Amperes range into the (common) anode line during the testing you can track the current through the Nixie tube while connecting the cathode pins or leads to GND - without needing to meddle around with the meter wires. The unused cathode pins are left open (the term "floating" is used often). You will be able to measure voltages up to U_a on the pins not connected.

Further advantage: if you have several Nixies in a circuit, these have all one common U_b wire. If you install a mA-Meter in that line you get the total current drawn for all nixies. And can assume that the individual current is total current divided by the number of tubes you are using. This is not *absolutely* true - but we won't win the Noble Prize with a very precise research on that anyway.

Some quick maths to calculate the values for the limiting resistor

$$U_{ra} = U_b - U_a \rightarrow 220 \text{ V} - 140 \text{ V} = \mathbf{80 \text{ VDC}}$$

$$R_a = U_{ra} / I_a \rightarrow 80 \text{ VDC} / 0.002 \text{ A} = \mathbf{40.000 \text{ Ohms}}$$

$$P_{ra} = U_{ra} * I_a \rightarrow 80 \text{ VDC} * 0.002 \text{ A} = \mathbf{0.16 \text{ Watts}}$$

Since there is no 40 KOhms resistor in the range of ordinary E24 5% standard resistors it will surely do if you pick a 43 KOhms type 0.25 Watts here, not to exceed the 2 mA cathode current.

Calculation for the Nixie Anode-Resistor

Supply Voltage U_b V
 Anode Voltage U_a V
 Cathode Current I_k mA
 U_{ra} : V
 R_a : K Ω
 P_{ra} : Watt

If you just press [Calculate] the values for the given U_b , estimated U_a and the given cathode current I_k are used and the output is the current across the anode resistor U_{ra} , the resistor value in Kilo-Ohm and the thermal loss P_{ra} of the resistor in Watt.

For your own calculation just overwrite the values in the upper 3 lines with what you need and then click on [Calculate] again.


220 VDC is quite a bit. How to get them *safely* ?

Well ... the professional approach is to have either a special transformer for the required voltages or at least an isolated 1:1 ratio separation transformer. If you live in the "low voltage" areas of the world where 110 VAC is the usual AC mains voltage you *may* survive a shock from the life wire. If you live in the "high voltage" areas like here in Germany the 230 VAC line voltage will surely kill you if you accidentally happen to be good grounded. A 1:1 transformer isolates the input voltage from the output voltage so you are not directly connected to AC mains. The 230 VAC that goes in comes out as 230 VAC - but you have no connection to Earth (GND) when touching any wire. You are -nonetheless- toasted if you touch *both* wires at one time.

The professionals phrase is "galvanically separated" - it is good to know that.

Separation transformers are usually big, heavy and expensive. Not as expensive as your life of course, but enough to blow a budget. In our case however we don't need Kilowatt capabilities. A few Watts will do - so we can build our own separation transformer by simply using two small transformers "Back to Back".

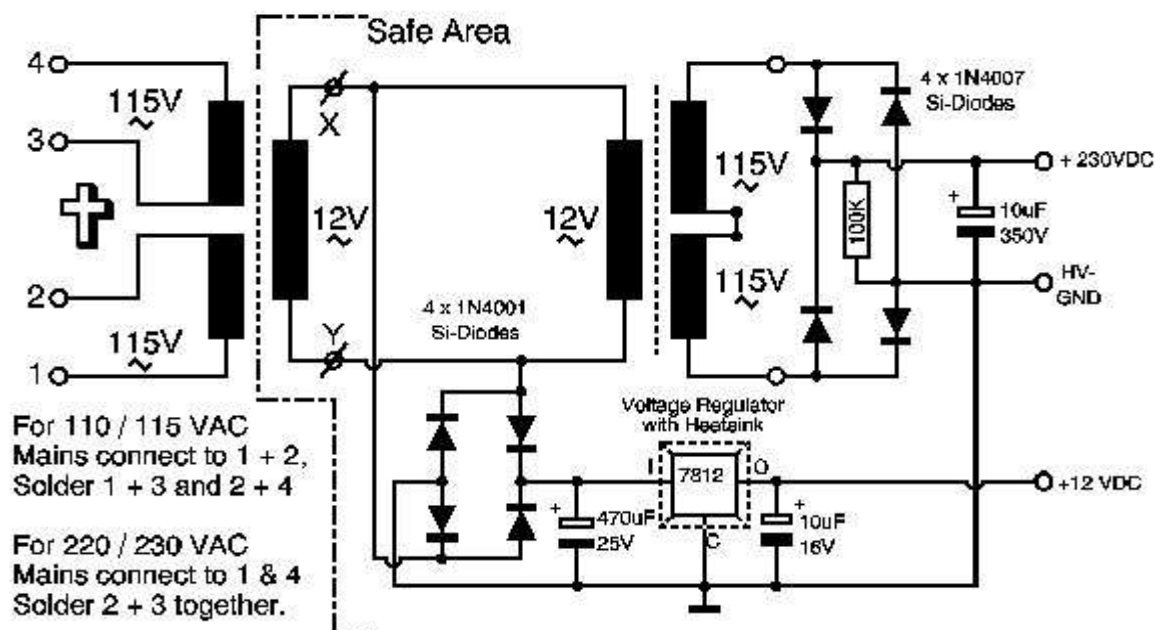The graphic below will show this simple solution.



The transformers can be simple, relatively cheap print-type transformers with greater 4 Watts output power. The ones I used on my prototype clock are rated 4 VA (Volt-Amperes) with a single 230 V primary input and a single 12 V / 300 mA output. If you cannot get those - take two with e.g. 15 VAC or two with 8 V AC. The "intermediate voltage" between the two is of lesser importance, it is used for the logic board only. But at least the "one on the right side" must have a 230 V coil.

If you have two different transformers: the bigger (stronger) one must be the one connected to AC-mains. You cannot run a 10 Watt transformer from a 5 Watt type back to back for example. The 10 Watt has a lower resistance for the secondary coil - and the 5 Watt secondary coil is then overloaded. At least when you add load to it. It may work for some time however, but not reliably.

The 4 diodes 1N4001 for the low voltage circuit can be replaced by a block rectifier like the B40-C1000 for instance; the 4 diodes 1N4007 for the high voltage part can be substituted by e.g. a B1000-C125 rectifier bridge. This rectifier(s) must be capable to run continuously with 350 V at least, so the *minimum* were a 1N4004 (rated 400V).

Other than that there are no secrets in that circuit. The 100 KOhms parallel to the 10 μ F / 350 V capacitor in the HV part helps - for safety - discharging the capacitor when no load is placed across the output. That's all. For your own pleasure you may add a 1 KOhms resistor at the +12V output and a red LED ... to remind you to the fact that the power supply is switched on.



With my two 4-Watt Transformers I get 15 V AC in idle between the transformers, 210 V AC idle voltage at the HV end. Also in idle the DC-voltages across the rectifiers are 18.5 V resp. 290 V DC. The high voltage however drops down to about 200 VDC when loaded with 4 x ZM1080 or 4 x ZM1020 Nixies and a total of 4.8 mA current drawn. A power supply built like that will suffice to play around with various types of Nixie tubes and get some insights on how they work.

Important: Security - and some useful hints

If you use a power supply like that above you *will* need a medium-blow 0.315 Amps fuse in one of the AC main wires for protection when -in the worst case- the transformer goes south. You should also install the whole power supply unit in a plastic case so that it is factually impossible to touch any AC-line wire. That unit shown above is a *prototype* not intended to be really used that way.

If you can get one of these "wall wart" transformers that have about 500 mA at 12V AC you are fine off. In this case you only need one transformer in the clock itself and a power socket where the AC-Adapter plugs to. For the above schematic the left-hand transformer is your external wall adapter and the AC-input socket connects to the points marked with "X" and "Y" then.

Some DC-Adapters can be reworked: if you can open the case of it without destroying it - just unsolder the diodes and the filter capacitor that can be found in most of them and connect the output wires directly to the secondary side of the transformer. Then you only need the part of the power supply further above that is right from the left (input) transformer. The 12 V AC (or 8 or 9 or whatever) comes from the wall-wart and your second transformer must be chosen accordingly. And -if you go lower- the 7812 must be replaced by e.g. a 7508 (8 V output) or 7805 (5 V output). The circuit itself doesn't care much when running with anything between +5 and +15 V DC.

If you opt for that solution you can make your clock case from "more dangerous material", like steel, copper, sheetmetal, carbon-fibre or anything else conductive. You don't have the AC line fed into the unit and the worst thing that can happen is, that you shorten your electronics elsewhere and it simply doesn't work -or- damages the transformer(s).

Okay - but why building a *clock* from these Nixies ?

Good question. Today you can pick a lot cheapo LCD clocks from supermarkets for a few bucks. But - how do they look ? Simply boring.

Go back to the Nixie animation further above. Look at it for a while and I'm sure you can spot the difference.

I built digital counters and clocks with LED 7-segment displays and 74xx TTL-chips already in the 70's. The commercial clocks used ready-made circuits, offered alarm and such, but they looked cheesy cheap - didn't match my taste - and those who did were horribly expensive. So I made my own desktop clock.

Same reason for the Nixie Clock: a custom-made case, antique looking glass tubes somewhere in it or placed on top - a wide variety of possibly creative, unusual designs. You can make it from all material you'd always wanted to build a clock from. Wood, steel, acrylic plastic. Transparent, translucent or granite-solid.


However: the Nixie Clock described here is *Just A Clock*. Not a stop watch, timer, alarm clock or anything like that. You *may* add some "Bells and Whistles", but due to the nature of the circuitry it might be a bit complicated. More on that later.

Getting started with it: the proper timing

Heart of any clock is a source for a timing signal. Cheap AC-powered alarm clocks use the 50 or 60 Hz AC line to generate a more or less accurate clock-signal from it. Usually that would do - given that the accuracy *over the whole year* on the AC-line is within a 1 % range. Nonetheless I'd decided not to use that. First reason was to be independent from the AC frequency. Secondly a crystal oscillator offers even better accuracy than line-AC and third I had a circuit at hand anyway

I used for a couple of applications in the past. Main advantage: it operates with a generic 32.768 KHz mini crystal widely available - and comes out with a 1 Hz timing pulse. The schematic below shows the circuit.

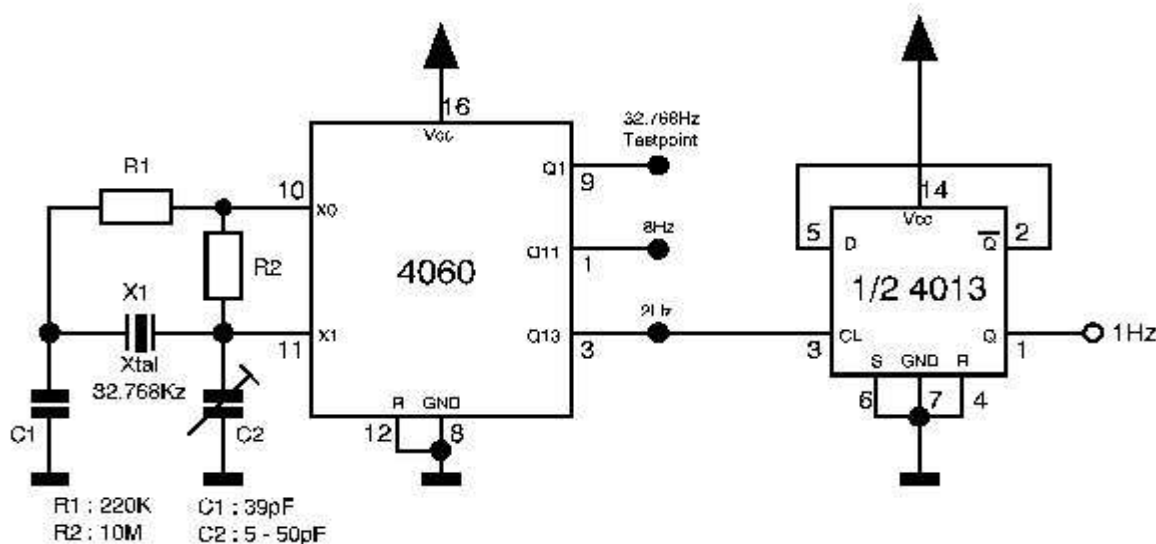Improved 1Hz-Generator for Nixie Clock Project



There are two resistors: R1 acting as current-limiting resistor and R2 bias resistor. This latter one is a) dependent to the circuit voltage applied to the 4060 divider chip and b) dependent to the current flow through the crystal and its capacity. I made good results with either omitting this one or using a 10 Mega-Ohms to start with. Your individual mileage may vary.

The crystal I used is a miniature clock crystal X1 in a round case with 19 pF internal capacity. The "tie-up" capacitor C1 is a low-loss ceramic type, the trimmer capacitor C2 is a standard plastic type. With a frequency counter connected to the 4060's pin 9 you can measure the buffered crystal frequency and adjust it to read exactly 32.768 Hz.



The 4013 RS Flipflop is used to divide the 2 Hz from the 4060 down to the 1 Hz base clock. The second half of the 4013 might be used to divide the 8 Hz signal at pin 1 down to 4 Hz for a "fast forward" set mode - not shown here however. If you are not using the second half of the 4013: tie the pins 8, 10 and 11 to GND and connect 9 and 12. Pin 13 stays open. If you decide to use the 4013 pin 11 is your input, 13 the output.

It is highly recommended to keep the wires of the components (caps and resistors) short trimmed and the leads between the components as short as possible. If the oscillator fails to start up or dies after several seconds: make the bias resistor larger. It may go up to 10 MOhm with these miniature crystals - or even left away. The bigger HC-style crystals with higher internal capacity may require 100 KOhm - 1 MOhm bias resistors. If you don't want a trimmer capacitor you may use a ceramic capacitor of the same value as C1 as well. Doesn't hurt the overall accuracy that much.

In the meantime - after I edited this page for the last time - I had built numerous oscillators with the 4060 and got a lot responses from other folks. Alternative concepts for the trimmer position,

values of R1 and R2 and the C1 and C2 have been discussed.

Usually you have a datasheet for the mini xtal X1 to start with. This datasheet shows the internal capacity - which *use to be* about 16 - 19pF.

The value for the tie-up cap C1 should be 2x the xtal capacity. 39pF fits quite nicely here.

The value for C1 should be [xtal capacity < C2 < 3x xtal capacity], where 5 - 50pF covers the entire range.

Determining the values for R1 and R2 is more tricky.

While R2 could be omitted in the best case for very dense packing of components R1 is essential for the clean function here. If it is too high the xtal fails to start - if it is too low the xtal enters "overtone mode" and the oscillator output frequency is either totally erratic or way higher than supposed.

For R1 220KOhm has proved to be a good value, R2 should be 10M. If you have xtals larger than these micro-types your R1 needs to be reduced - down to 2K2 for a HC32 xtal and R2 might be reduced to 4M7 for stable operation.


The 4060 allows to run at up to 4MHz @ 15V supply. If you have too much room and wouldn't care about two more 4017 dividers: pick a 3.2768 MHz xtal, leave R1 away or reduce it to 2K2, R2 to 10M, C1 to 22pF and install a 2 - 22pF trimmer. You get 200Hz at the Q13 - divided by 2 in the 4013 for 100Hz. Add two more 4017s and you are again at 1Hz with -probably- higher stability due to the higher reference frequency. However: you should not test the 4060 frequency at pin 9. The probe capacity will alter the result. You should test at O4 (pin 7) and your counter should read 204.800 Hz. The trimmer allows a change of about +/- 25 Hz. If you don't have one adjust C2 to the center, where about the half of the static "leafes" are visible. That will do to for most cases.

Step by Step: the dividers (Seconds, Minutes and Hours)

At that point we've got to hold for a moment and think about a basic design question:

"Do we want a seconds display or only minutes and hours ?"

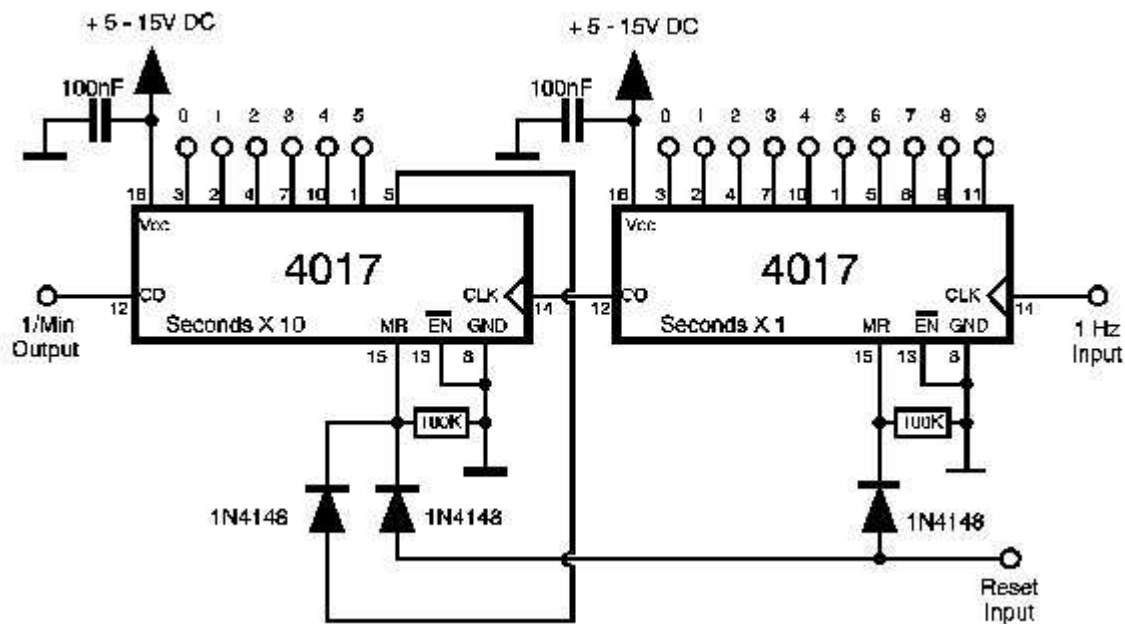In either case we need two 60-stage dividers. Building a clock without a seconds display saves room and driver transistors. Let's have a look at this part of the circuit.




The CMOS chip 4017 is a "5-stage Josephson decade counter" with built-in code converter. Each low-to-high transition (= "positive edge") on the clock input 14 advances the counter one position up from Q0 to Q9, which go to high level then. A logical "1" signal on the reset input 15 sets it back to Q0.

To count the seconds properly we have to pull the first counter reset to GND with a 100K resistor, which causes the counter to count from 0 to 9 with every clock signal. At 9 it jumps back to 0 with the next clock pulse and the "Carry Out" signal at pin 12 changes from "0" to "1", which counts the second counter one position up. The second counter has the Q6 output wired to the reset pin. After the 59th clock pulse it jumps back to "00". Any of the "Carry Out" signals changes back from "1" to "0" after receiving the positive edge of the 6th clock pulse.


The capacitors on each pin 16 are local buffer caps only. They are there to reduce the effect of local voltage sags. This is mainly an issue when the circuit is built on experimental board or with no board at all. Given you have a stable, clean supply voltage it will surely suffice to leave them away or add one or two of them on the chips farthest away from the point where the supply voltage is fed into the circuit.

The "100nF" rating seems to be a tad uncommon to some people. It has been brought to my attention that it may lead to some confusion and I had been asked if I meant "microfarad" instead (but didn't have the proper sign). No - it is Nanofarad. Or - alternatively - I could use "0.1 μ F" here to clarify what I meant.

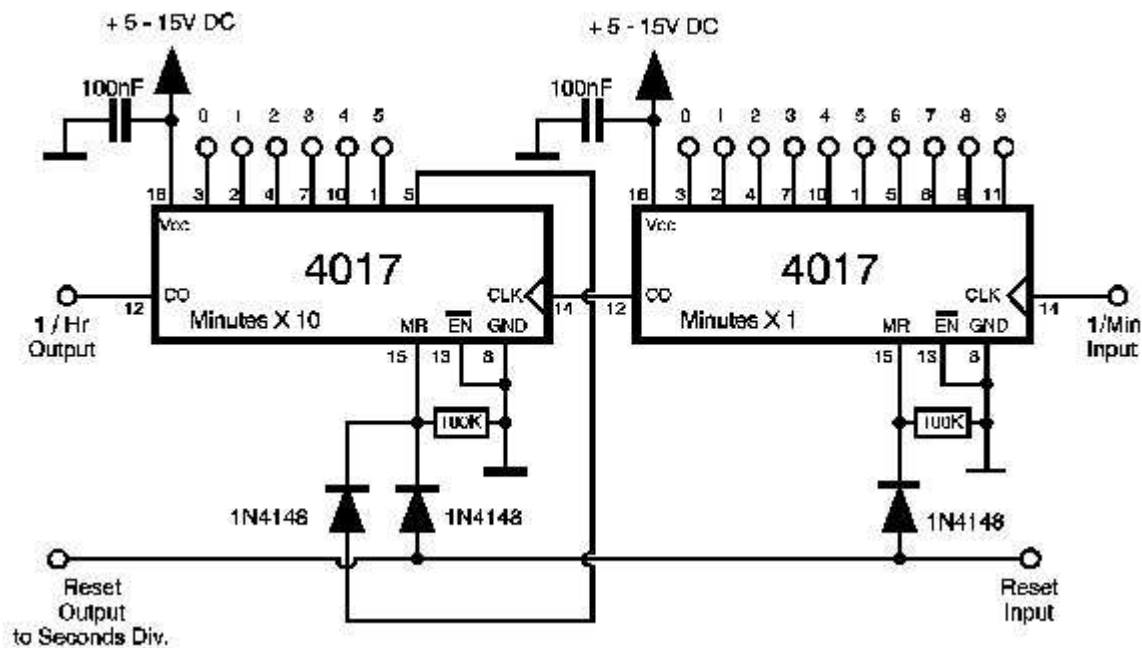The Seconds Divider is followed by the Minutes divider. Looks in most of it like the Seconds Divider - but the In and Out is named different. Functionally they are alike.



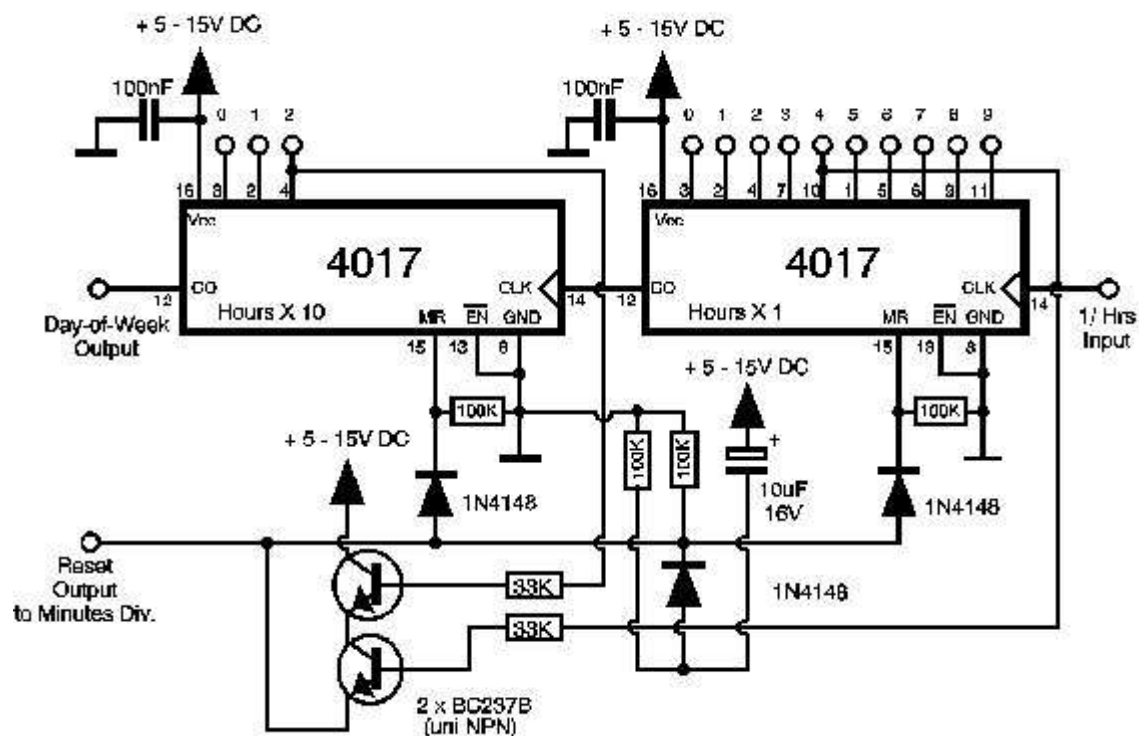Now comes a tricky part. In Europe (where I live) we have a 24-hours display. We're not "AM/PM" guys over here. 24 is a bit hard to decode, since it is neither a roll-over nor is it just a single digit rollover. So note the reset-logic here. It is a wired-AND with 2 NPN-transistors that pull the Master Reset up when a "4" appears in the LSB while there is a "2" on the MSB hours display. Neat, eh ?




Also note the 10 μ F capacitor, the 1N4148 diode and the 100K resistor. These three form the

The carry-out signal from the last counter might be used to create a "Day of Week" display with another 4017 and e.g. a backlighted frontpanel. Be creative.

The counting on the hours display does not start at 00:00 but at 01:00. All numerals need an offset. The Q0 output sets the "1", the Q1 output the "2" and so forth. Due to that you have to move the input of the 10-hours from the "Carry Out" (pin 12) to the pin 11, which advances the 10-hours with every transition from "9" to "0".

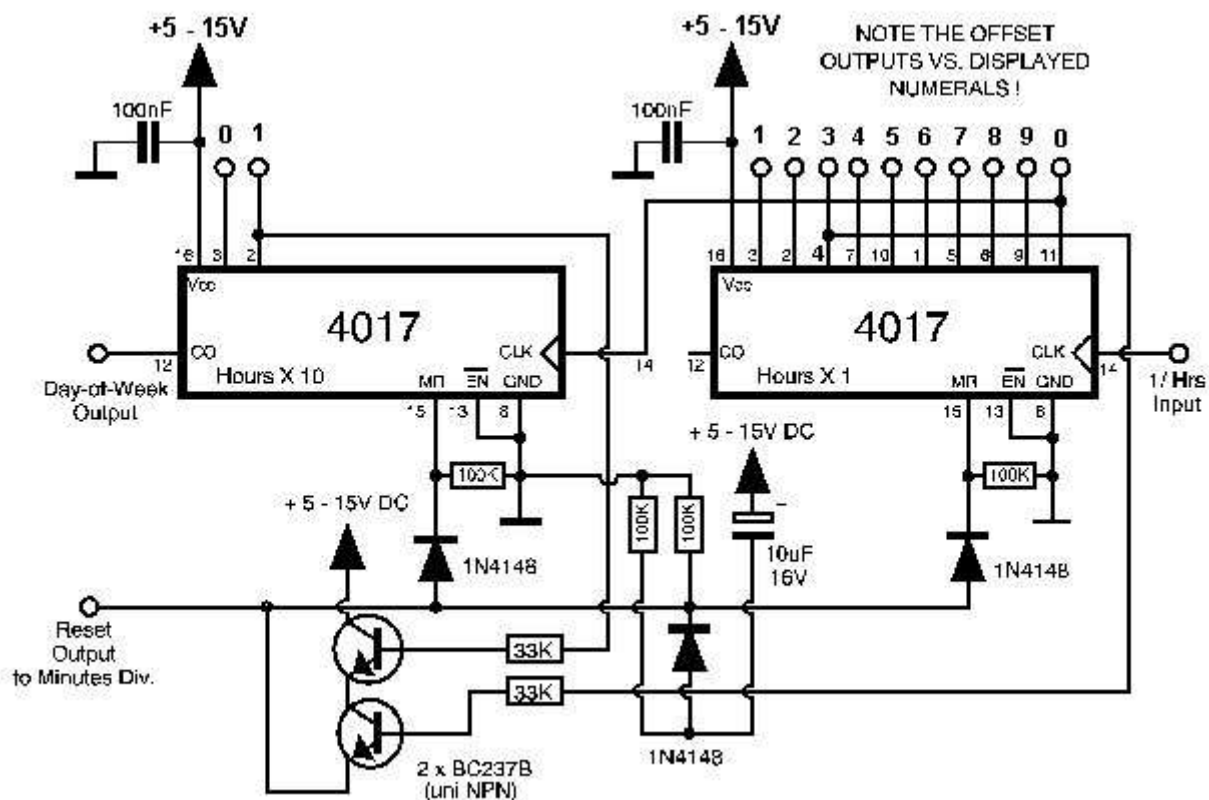While the counting resets at one minute after "12:59" at "13" in the hours display (and not at "24" after "23:59") you need to alter signal for the Wired-AND to the reset the hours stage to pin 2 on the 10-hours and pin 4 on the 1-hours.



Problem with the Nixies is the relatively high voltage they operate with. Each cathode pin that is not grounded is pulled up due to the electron migration inside the gas-filled tube to near the anode voltage U_a . This may be 140 VDC - or above on some types. A circuit that pulls down a cathode from this "idle voltage" to GND must be capable to handle it. If you use a NPN transistor the Emitter (E) is tied to GND and the Collector (C) is connected with one of the cathode pins. The Base (B) is connected to the counter outputs via an appropriate current-limiting resistor. The "Collector / Base Voltage with open Base" U_{cb0} specs for the transistor must be higher than the idle voltage on the cathodes. That's the voltage a transistor can handle when being not conductive


(= not switched on). This disqualifies most common transistors, since their U_{cb0} is only 15 - 60 Volts.

But - there are matching transistors available. Namely those designed for TV-purposes (video stage, color final stage, deflection circuits) or various HF and switching transistors can be used. If you have access to a listing of transistors with their base data you will easily find some matching types. Most common and low-cost transistor is the MPS-A42, which is a NPN transistor with $U_{cb0} = 300\text{ V}$, $I_c = 0.5\text{ Amp}$ and $P_{tot} = 0.625\text{ Watts}$ designed for TV video stages. In Germany we pay 0.08 Euro (about 7 cents) for one - comes cheaper if you buy 100 for example.

Also useable are BF118, BF179C, BF259, BF338, BSS48, BUW37 (all with a metal-can case) or BF413, BF420A, BF422A, BF483 (plastic case), AT1, AT2, DC or NMPSA-42 (SMD types) to name a few.

Alternatively you could tie down all cathodes to GND with a resistor of 100 KOhms to reduce the idle voltage - without starting the cathodes to glow already. In this case a more versatile transistor with a U_{cb0} of least 65V like the BC174B or BC546 or BC846 should do. However - you need 3 times more resistors.

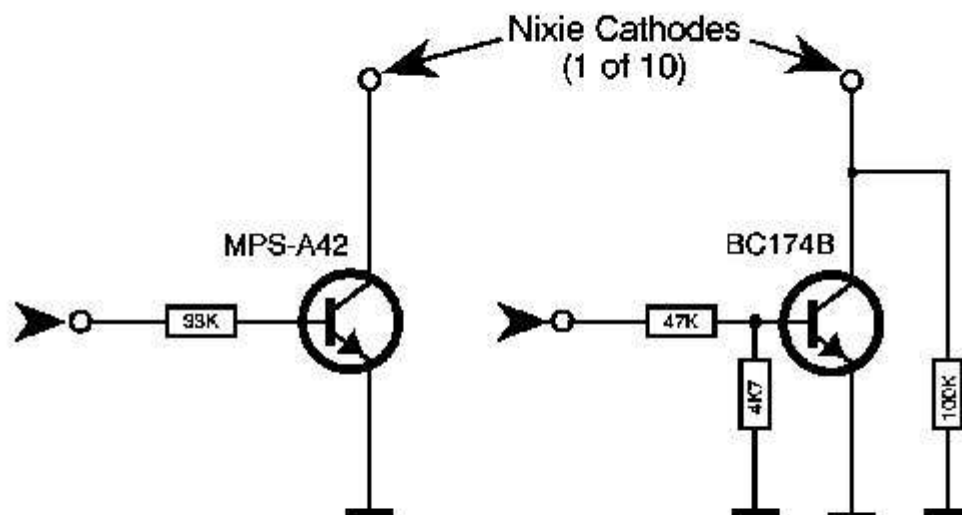The schematic below explains the different driver circuits.



The left circuit is the pure simplicity: only one 33 K resistor between the counter output and the base of the transistor. While in the circuit on the right you have an additional voltage divider with a 47 K / 4.7 K resistor between the counter output and the base plus an additional 100 K "pull down" resistor that reduces the voltage between the turned-off cathode and GND.

To tell the truth: I didn't bother much with the circuit on the right side. In fact I got the idea from an old TV program display circuit that uses Nixie tubes. But the MPS-A42 transistors are fairly cheap and there's no need to switch to some low(er) voltage types, which aren't much cheaper - if at all. But maybe you happen to have several hundreds of them around ... feel free to use them.

The circuit itself is simple: the positive signal from the counter output passes the current-limiting


33 K resistor and turns on the Collector-Emitter path, which then grounds the cathode pin of the nixie. This turns on the neon glow for that cathode.

Under Control: Switches for setting the clock

Since this clock is only a counter it does not get the time "by automatic". However: since it has "Auto-Zero" function you could try plug it in at midnight exactly ...

So we need switches. I like clocks where minutes and hours can be set independently. And which has *not* to cycle through the entire 24-hours-counting in fast forward and then set the "finetuning" with a slow mode switch. I prefer setting the minutes, then the hours. Once I goof on that I don't need to re-run once again. And again. Maybe.

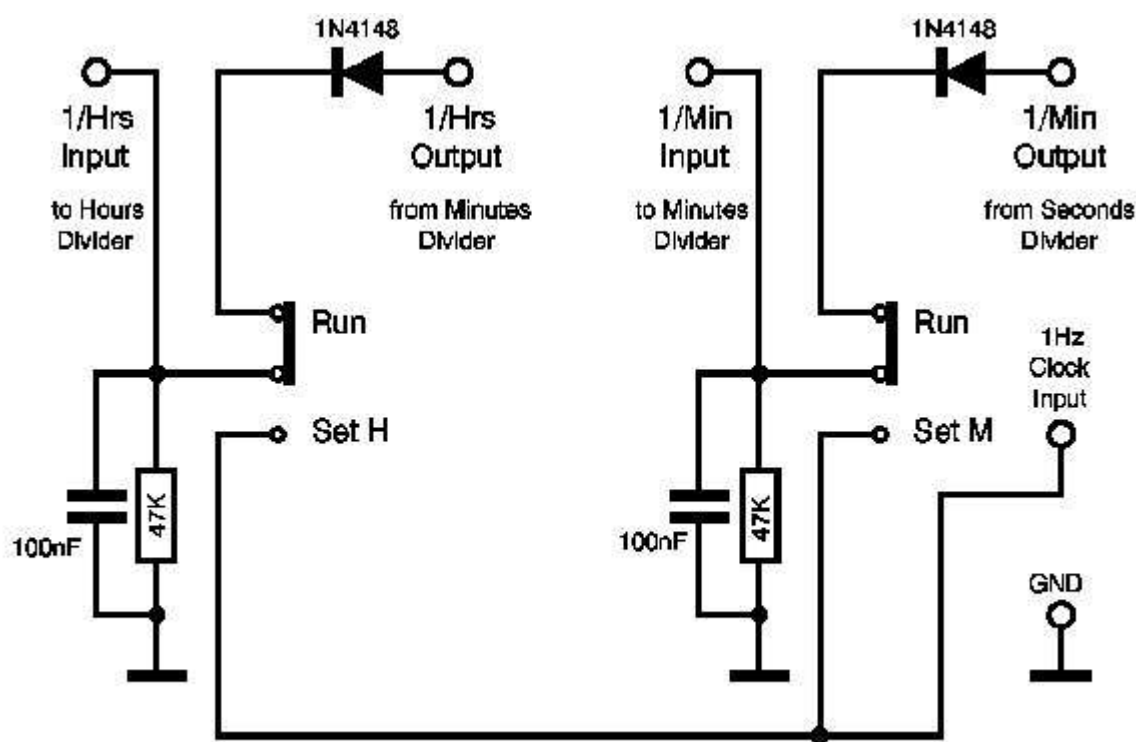The solution is pretty simple. Two toggle switches, one between the seconds and minutes divider and one between the minutes and hours divider will do the trick. Look here:



The common contact on either switch is connected to the input of the counter to set (minutes or hours). The resistor / capacitor combination debounces the switch a bit to avoid "scrolling" when switching back from set to run mode.

The upper (NC - now closed) contact is connected with the output of the previous counter. The Diode is for decoupling. It is not always necessary, but might help avoiding problems, when the switch has "take-over" contacts that close *both* contacts momentarily while toggling.


The lower (NO - Now open) contact is connected with the 1 Hz base clock from the 1Hz-Generator. If the clock is too slow for your feel (especially on the minutes count-up) feel free to use the 2 Hz from the Pin 3 (Q13) of the 4060 directly or even use the 4 Hz signal that can be generated from pin 1 (Q11) of the 4060 and the second half of the 4013 Flip-Flop. Or use pin 2 (Q12) on the 4060, which offers 4 Hz already.

Ticking the seconds: A blinking colon

Those who opted to build a 4-digit clock with Hours and Minutes only (and save 16 transistors and 16 resistors at least) may wish to have something that indicates the seconds pacing on. Analogous to the odd blinking ":" on other digital watches.

Easy done. If your Nixie has a decimal point you could use one of those. Nixies that have a decimal point to the right of the number should use the one in the 1 / Hours digit (LSB), with a left-side decimal point you use the one in the 10 / Minutes digit (MSB). No special treatment required. The anode current on the Nixie goes up a bit - but that shouldn't harm anything.

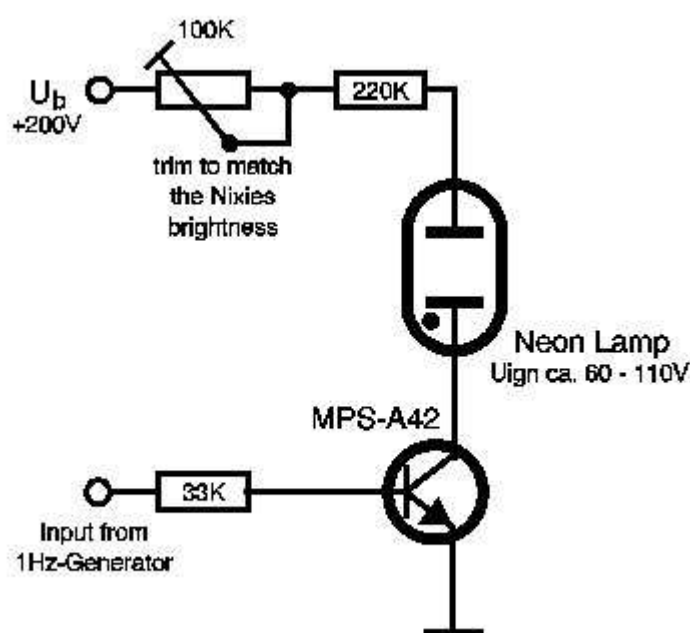Those who use Nixies without decimal points or aren't attracted much by the look may use a single neon-lamp in the middle between the hours and minutes display. See the schematic below.




This is how the single, middle flashing neon lamp looks on my second prototype: it is a relatively long and slim lamp I recovered from some electronic crap in the early 70s ... almost 3 decades later it came handy to act as a blinking colon in a home-made Nixie Clock. Life *is* funny.

You could also use a LED - or some "Magic Eye" tube that alters height / angle during the seconds ticking. But "real tubes" require a heater supply which is several 100 mA normally - while the entire circuit with the 8 CMOS chips, the driver transistors and such takes less than 10 mA. The Nixies take another 5 mA from the 220 V supply - and that's all. If you stuff in a "radio tube" you will have to extend both: your low-volt and high-volt supply as well. So far you come away with about 6 Watts electric energy - given that the two transformers have an efficiency of about 80 %.

Bells and Whistles: Adding extra-functions

(Not yet fully approved)

An easy method to add an extra function is using an integrated sound circuit. Usually these chips are positive-edge triggered. Means: you pull the input high and the sound plays. Given you got a chip with a "Big Ben" bell tone you simply add an AND-gate output (or two transistors as for the "Hours" reset circuit) to the sound-chip "activate" input. The AND-gate input is connected with the "0" outputs (pin 3) on the minutes divider 4017s.

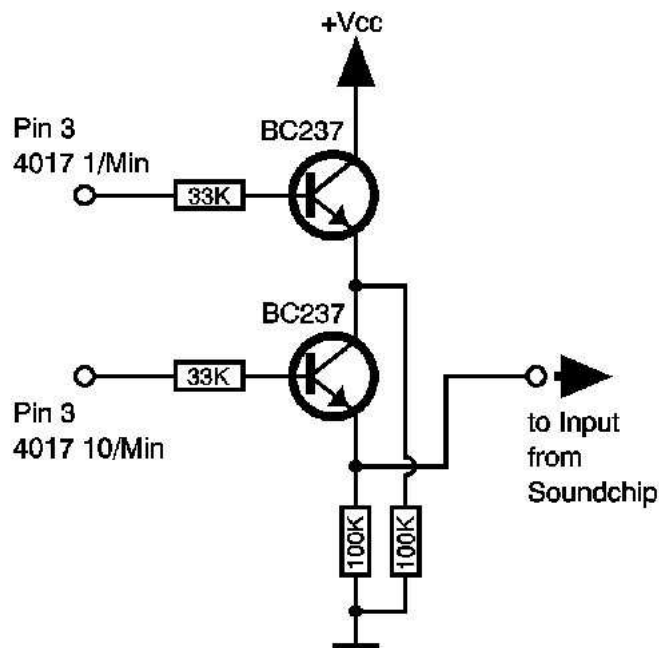

Result: any full hour when the display jumps to "00" in the minutes the sound is triggered.
Hint: include a switch to shut off the sound. Sometimes these "good" ideas turn out to be somewhat enervating on the long run. (Big Grin !).

Finally: some pictures from my prototypes

So far I made three different prototypes. After some testings and trials the circuit has stabilized to the components shown above. There is however a lot room for improvements or changes, additions and whatnot. Especially the switches for setting the time are subject to permanent change. A printed circuitboard is also (yet) missing, but I'm working on it.

Here are some pictures of the two working clocks.



The 1Hz generator.
Built as sample, used in "Study" clock.



6 x ZM1040 in red.
30mm character height.
Mounted 30° to the right.
Rail was for ZM1020 originally.



A standard sized Euro-Board.
The red LED takes more
power than all the chips.



A case study with 4 x Z5600M.
(ex-GDR ZM1020-equivalents)
Just completed.



Not enough room ?
Build it compacter.
That's how I did it.



Everything on very
small boards. To fit in
the "Study" case.



Still without the neon lamp
in the middle.
The Nixies were ZM1080,
but I removed the red filter.



The "air-wires" phase.
Switches not installed.



Stacked board and display.
Different switches now.



A divider / driver circuit.
Very compact built.
One of two.

A look inside.
Yes - it is pretty tight filled..

Other related Topics:

[My Nixie Tube Mini-Tester - My Little Nixie Collection](#)
[A "7-Segment-To-Nixie" Decoder \(very strange thing\)](#)
[Dimming the Nixies - A Nixie Clock For Everyone ... !](#)

© 2001 by [Peter H. Wendt](#)

Maintainer Notes: all tips given in this document are without any warranty.

If you accidently kill yourself, burn the house or blow everything - your problem.

Switch your brain on, think, reconsider and *then* act. But first: **Think !**

You may however pick anything you like from this page if you quote the original source.

Feel free to leave me a note, reports, pictures or ask questions if you like.

I try to respond if my time allows, which is not always the case.

Sorry. I have a lot hobbies and a job.